

CMOS Design Project: 4 Bit Odd Parity Checker



Indian Institute of Information Technology,

Nagpur

ECL 312: CMOS Design

A Project Report on: 4-Bit Odd parity checker using CMOS

Submitted By:

Aman Kaliramna (BT22ECE101)

Submitted to :

Prof. Paritosh Peshwe

Department of Electronics and Communication

Project Overview

This repository contains the design and simulation of a 4-bit odd parity checker implemented using CMOS technology. The project includes the complete circuit design, simulation using `ngspice`, and layout implementation using Microwind under 90nm technology. The odd parity checker is a fundamental component in error detection systems, ensuring data integrity by verifying whether the number of 1's in a 4-bit input is odd.

Objectives

1. Design and simulate a 4-bit odd parity checker using CMOS technology.
2. Create and verify the **NgSpice netlist** for circuit simulation.
3. Implement the physical layout using **Microwind** in **90nm technology**.
4. Analyze and verify the circuit's performance through simulation results

Design Description

Circuit Operation


- Takes **4 input bits** (A, B, C, D)
- Produces a **parity bit** output (P)
- P can be compounded as $P=A\oplus B\oplus C\oplus D$ where \oplus denotes XOR logic
- Output $P = 0$ when number of 1's in input is even (to make total number of 1's odd)
- Output $P = 1$ when number of 1's in input is odd

Logic Implementation

The circuit implements the following logic:

- Uses **XOR gates** to check for odd/even number of 1's
- Implemented using **transmission gates** instead of conventional CMOS design for minimal area occupation.

Transmission Gate Circuit:

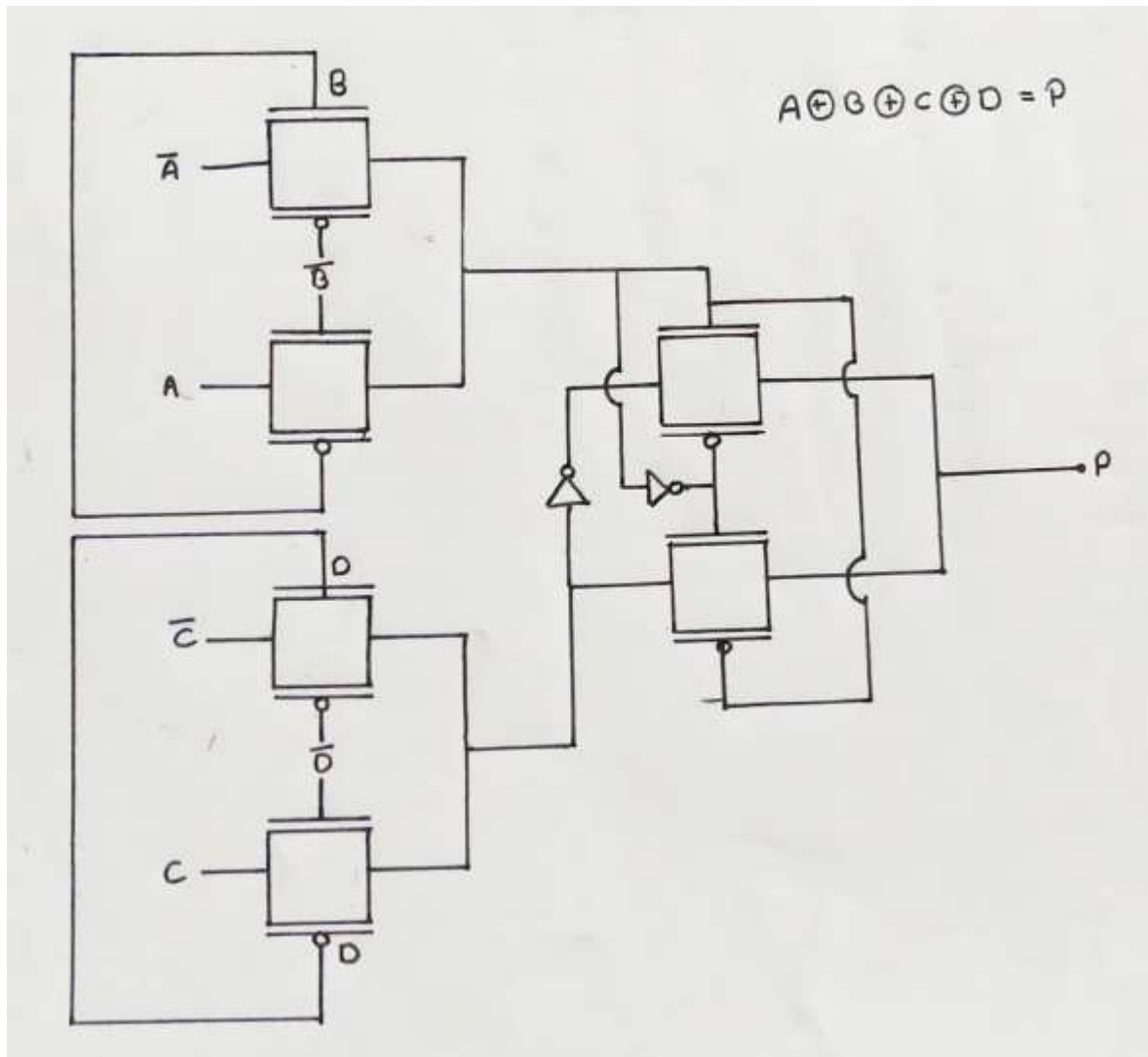

Simulation Files

Below are snippets of the circuit files used for simulation in **ngSpice**:

ngspice circuit file:

****4 Bit Odd Parity Checker****

```
.model nmod nmos level=54 version=4.7
```

```
.model pmod pmos level=54 version=4.7
```

```
.subckt inverter in vdd out
M1 out in 0 0 nmod w=100u l=10u
M2 out in vdd vdd pmod w=200u l=10u
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.ends
```

```
.subckt tg in out sel selb
M1 out sel in in nmod w=100u l=10u
M2 out selb in in pmod w=200u l=10u
.ends
```

```
.subckt xor_gate a b out ab bb
Xab_b a out b bb tg
Xa_bb ab out bb b tg
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.ends
Va 1 0 pulse(0 5 0 0 0 50m 100m)
Vb 2 0 pulse(0 5 0 0 0 100m 200m)
Vc 3 0 pulse(0 5 0 0 0 200m 400m)
Vd 4 0 pulse(0 5 0 0 0 400m 800m)
Vab 5 0 pulse(5 0 0 0 0 50m 100m)
Vbb 6 0 pulse(5 0 0 0 0 100m 200m)
Vcb 7 0 pulse(5 0 0 0 0 200m 400m)
Vdb 8 0 pulse(5 0 0 0 0 400m 800m)
```

```
Vdd 9 0 dc 5
```

```
* For Testing the following value should output ON *
```

```
Va 1 0 dc 0v
```

```
Vb 2 0 dc 0v
```

```
Vc 3 0 dc 0v
```

```
Vd 4 0 dc 5v
```

```
Vab 5 0 dc 5v
```

```
Vbb 6 0 dc 5v
```

```
Vcb 7 0 dc 5v
```

```
Vdb 8 0 dc 0v
```

```
Xab 1 2 10 5 6 xor_gate
```

```
Xcd 3 4 11 7 8 xor_gate
```

```
Xab_inv 10 9 12 inverter
```

```
Xcd_inv 11 9 13 inverter
```

```
Xabcd 10 11 14 12 13 xor_gate
```

```
Xout 14 5 15 inverter
```

```
.tran 0.1m 400m
```

```
.control
```

```
run
```

```
plot v(1) v(2) v(3) v(4) v(14)
```


```
plot v(14) v(15)
```

```
.endc
```


```
.end
```

Ngspice Output:

For DC input:

 


For pulse input:

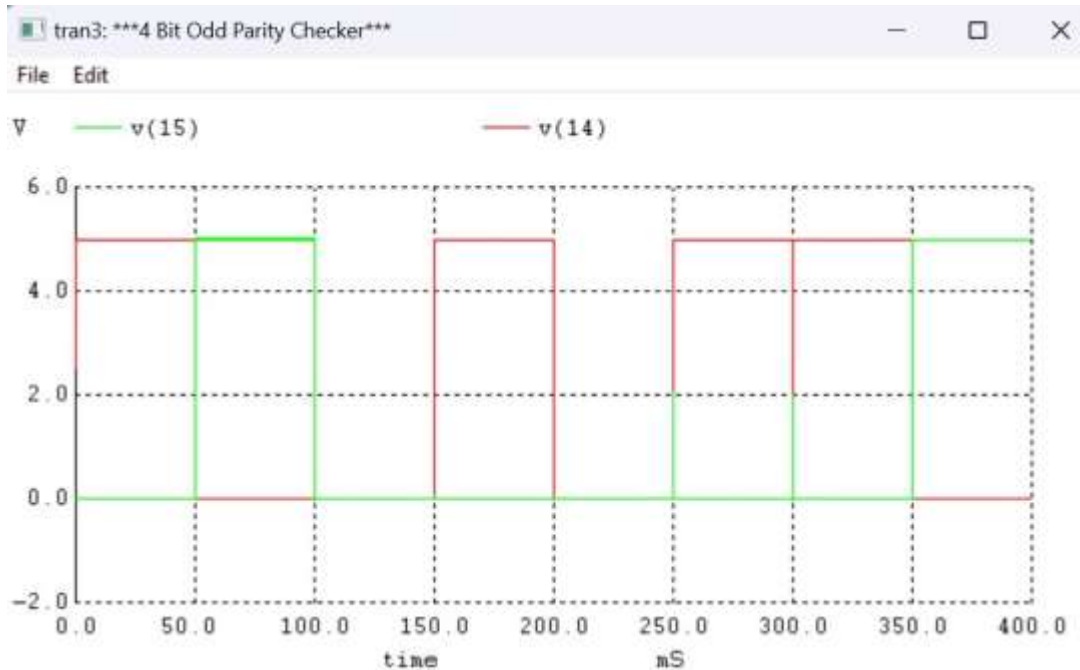


Layout and Waveforms

Circuit Layout:

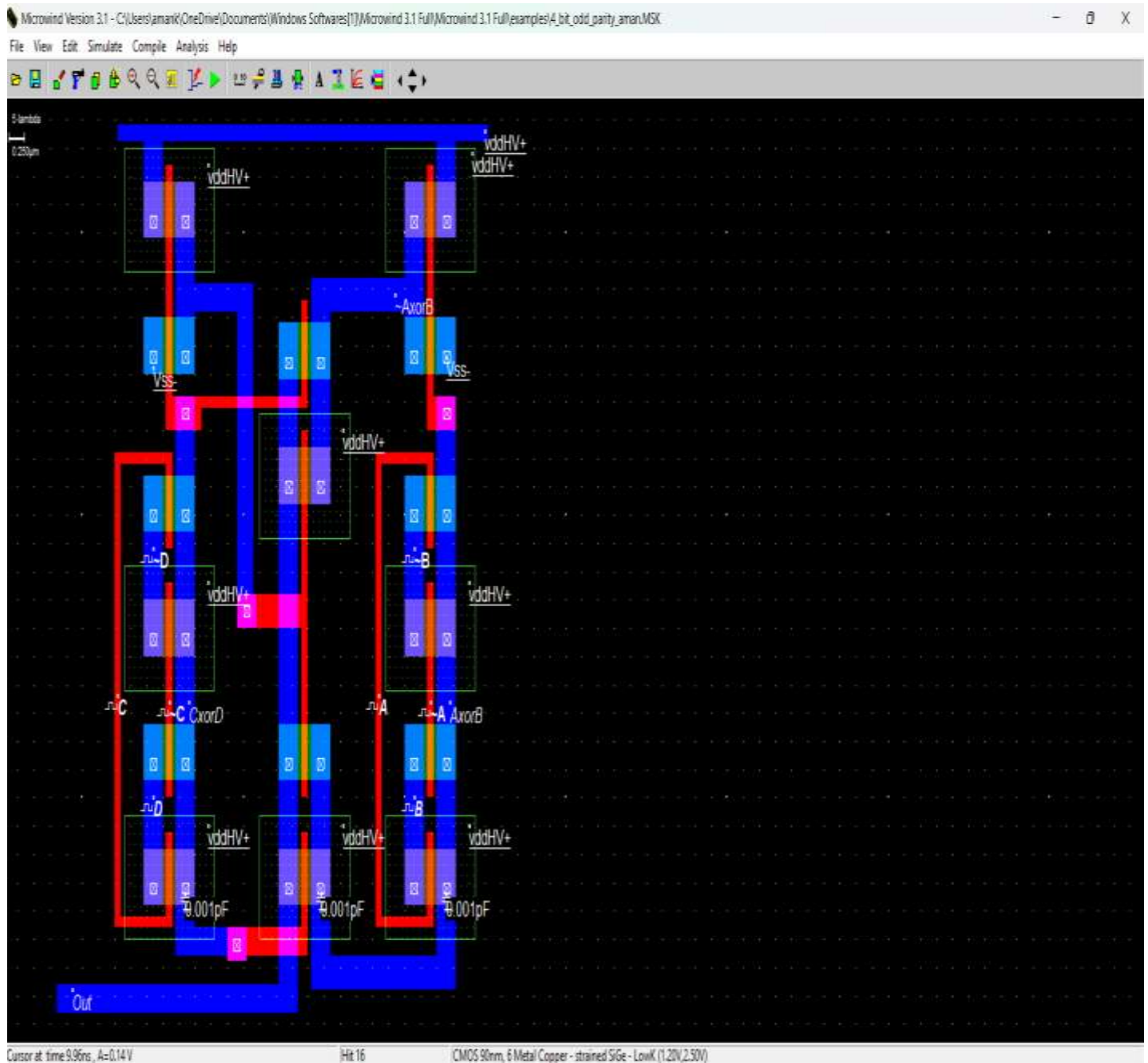

Output Waveforms:

 

Why Transmission Gates Over Pass Transistors?

The choice of transmission gates over pass transistors in this design was motivated by several key advantages:

- Voltage Level Preservation:
 - Pass transistors suffer from threshold voltage drop (NMOS passes weak '1', PMOS passes weak '0')
 - Transmission gates combine NMOS and PMOS transistors to ensure full voltage swing
 - This results in stronger logic levels and better noise margins
- Speed and Performance:
 - Pass transistors have asymmetric switching speeds (faster for one transition than the other)
 - Transmission gates provide balanced switching characteristics
 - Results in more predictable timing and better overall circuit performance
- Power Efficiency:

- Pass transistors may require additional buffers to restore voltage levels
- These buffers consume extra power and increase circuit complexity
- Transmission gates eliminate the need for voltage restoration, reducing power consumption
- Reliability:
 - Pass transistors are more susceptible to noise and voltage variations
 - Transmission gates provide better immunity to noise
 - More reliable operation across different operating conditions
- Layout Considerations:
 - While transmission gates use more transistors than pass transistors
 - The elimination of voltage restoration circuitry often results in comparable or better area efficiency
 - Simpler integration with other circuit components

Implementation Challenges and Solutions

1. Signal Routing Complexity

Challenge:

- Complex interconnections between multiple XOR gates visible in the layout
- Multiple crossing paths for signals A, B, C, and D
- Risk of signal interference due to dense routing in central area
- Need to maintain consistent delay across all input paths

Solution:

- Implemented a systematic routing strategy using different metal layers
- Used blue metal lines for main signal routing and red metal lines for cross connections
- Placed transmission gates in a symmetric pattern to minimize routing congestion

- Added strategic vias (marked with crosses in layout) to ensure proper layer connections
- Maintained equal path lengths for signals to avoid timing mismatches

2. Output Signal Stability

Challenge:

- Simulation waveforms show potential glitches during input transitions
- Multiple signal transitions need to be handled simultaneously
- Risk of incorrect parity output during simultaneous input changes
- Need for stable output across all 16 input combinations

Solution:

- Added 0.001pF capacitors (visible in layout) for output stabilization
- Implemented proper sizing of transmission gates (shown by gate dimensions in layout)
- Used balanced power distribution (vddHV+ routing) across the circuit
- Ensured proper ground (Vss-) connections for stable reference
- Verified functionality through comprehensive simulation (as shown in waveform)

Future Work

Potential improvements and extensions could include:

1. Extending the design to handle 8-bit inputs
2. Optimizing the circuit for lower power consumption
3. Implementing error correction capabilities

Conclusion

This project demonstrates the successful implementation of a 4-bit odd parity checker using CMOS technology. The design achieves:

- Correct functionality verified through simulation
 - Implementation in 90nm technology
 - Use of transmission gates
-